

BAPATLA ENGINEERING COLLEGE
OOPS AND PSPICE LAB (EC352)



PREPARED BY

CHESTI ALTAFF HUSSAIN M.Tech

Lecturer

&

M.RAJANI DEVI M.Tech

Lecturer

Department of Electronics and Communications Engineering
Bapatla Engineering College
(Affiliated to Acharya Nagarjuna University)
Bapatla-522101
2009-2010

LIST OF PROGRAMS

PROGRAMS BASED ON OOPS

1. Arrays 3
2. Pointers4
3. Console I/O Operations5
4. Objects and Classes6
5. Operator Overloading7
6. Function Overloading8
7. Inheritance9
8. File I/O Operations10
9. Virtual Functions11

PROGRAMS BASED ON PSPICE

1. Verification of Half-Wave and Full-Wave Rectifier	.. 13
2. Frequency Response of CE Amplifier	..15
3. Frequency Response of CS Amplifier	..17
4. Design of Wein-Bridge Oscillator	..19
5. Design and Verification of Class-A Power Amplifier	..21

PROGRAMS BASED ON OOPS

1. A C++ Program on Arrays.

```
#include<iostream.h>
#include<constream.h>
class ac
{
    private:
        char name[15];
        int acno;
        float bal;
    public:
        void read()
        {
            cout<<"name,acno,bal";
            cin>>name>>acno>>bal;
        }
        friend void showbal(ac);
};
cout<<"bal"<<a.bal<<"name"<<a.name<<"acno"<<a.acno;
}
int main()
{
    ac k;
    k.read();
    showbal(k);
    return(0);
}
```

2. A C++ Program on Pointers.

```
#include<iostream.h>
#include<constream.h>
class bill
{
public:
int qty;
float amount,price;
public:
void getdata(int a,float b,float c)
{
qty=a;
price=b;
amount=c;
}
void show()
{
cout<<"quantity="<<qty<<"\n";
cout<<"price="<<price<<"\n";
cout<<"amount="<<amount<<"\n";
}
};
int main()
{
clrscr();
bill s;
bill *ptr=&s;
ptr->getdata(45,10.25,450);
(*ptr).show();
return 0;
}
```

3. A C++ Program to illustrate the concept of Console I/O Operations.

```
#include<iostream.h>
#include<conio.h>
void main()
{
    cout.fill('/');
    cout.width(20);
    cout<<"well";
    cout.fill('_');
    cout.width(20);
    cout<<"done" ;
    cout.precision(2);
    cout<<113.5678;
    cout.fill('=');
    cout.setf(ios::right,ios::adjustfield);
    cout.width(20);
    cout<<"figure"<<"\n";
    cout.setf(ios::left,ios::adjustfield);
    cout.width(20);
    cout<<"figure"<<"\n";
}
```

4. A C++ Program on Objects and Classes.

```
#include<iostream.h>
#include<conio.h>
Class amount
{
Public;
Int number;
Float bal;
Display()
{
Cout<<"account number "<<number<<endl

Cout<<"account balance "<<bal<<endl
}
}
Main()
{
Account raja;
Raja.number=1245;
Raja.balance=2435;
Raja.display();
Account kumar;
Kumar.number=4564;
Kumar.balance=5677;
}
```

5. A C++ Program on Operator Overloading.

```
#include<iostream.h>
#include<constream.h>
#include<conio.h>
class num
{
    private:
        int a,b,c,d;
    public:
        num(int x,int y,int z,int w)
        {
            a=x;b=y;c=z;d=w;
        }

        void show(void);

        void operator-();
};
void num::show()
{
    cout<<"\na:"<<a<<"\n b:"<<b<<"\n c:"<<c<<"\n d:"<<d;
}
void num::operator-()
{
    a=-a;b=-b;c=-c;d=-d;
}
main()
{
    clrscr();
    num x(2,2,8,4);
    cout<<"before negation:";
    x.show();
    -x;
    cout<<"\n after negation:" ;
    x.show();
    return 0;
}
```

6. A C++ Program on Function Overloading.

```
#include<iostream.h>
#include<constream.h>
#include<conio.h>
Int sqr(int);
Float sqr(float);
Main()
{
Int a=8;
Float b=3.16
Cout<<"square ="<<sqr(a);
Cout<<"square="<<sqr(b);
Return(0);
}
Int sqr(int x)
{
Return(x*x);
}
Float sqr(float y)
{
Return(y*y);
}
```


7. A C++ Program on File I/O Operations.

```
#include<iostream.h>
#include<fstream.h>
#include<conio.h>
int main()
{
    clrscr();
    char name[20];
    int age;
    ofstream out("text");
    cout<<"name";
    cin>>name;
    cout<<"age:";
    cin>>age;
    out<<name<<"\t";
    out<<age<<"\n";
    out.close();
    ifstream in("text");
    in>>name;
    in>>age;
    cout<<"\n name:"<<name<<"\n";
    cout<<"age"<<age;
    in.close();
    return
    0;
}
```

8. A C++ Program on Virtual Functions.

```
#include<iostream.h>
#include<constream.h>
class first
{
int b;
public:
first()
{
b=10;
}
virtual void display()
{
cout<<"\nb:"<<b;
}
};
class second:public first
{
int d;
public:
second()
{
d=20;
}
void display()
{
cout<<"\nd:"<<d;
}
};
void main()
{
clrscr();
first f;
second s;
first *pt=&f;
pt->display();
pt=&s;
pt->display(); }
```

9.A C++ Program on Inheritance.

```
#include<iostream.h>
#include<constream.h>
#include<conio.h>
class A1
{
protected:
    char name[20];
    int age;
};
class A2:public A1

{
protected:    float height;
               float weight;
};
class A3:public A2
{
protected:char sex;
public:
    void get()
    {
        cout<<"name:" ;
        cin>>name;
        cout<<"age:";
        cin>>age;
        cout<<"sex";
        cin>>sex;
        cout<<"height";
        cin>>height;
        cout<<"weight";
        cin>>weight;
    }
    void show()
    {
        cout<<"\n name:" <<name;
        cout<<"\n age:"<<age;
        cout<<"\n sex:"<<sex;
        cout<<"\n height:"<<height;
        cout<<"\n weight:"<<weight;
```

```
    }  
};  
void main()  
{  
    clrscr();  
  
    A3 x;  
    x.get();  
    x.show();  
}
```

PROGRAMS BASED ON PSPICE

1. Verification of Half-Wave and Full-Wave Rectifier

AIM: To Verify the characteristics of Half-Wave and Full-Wave Rectifier.

CIRCUIT DIAGRAMS:

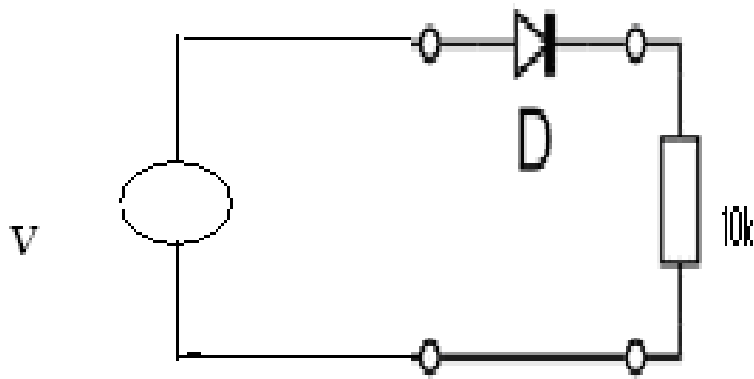


Figure1: Half Wave Rectifier

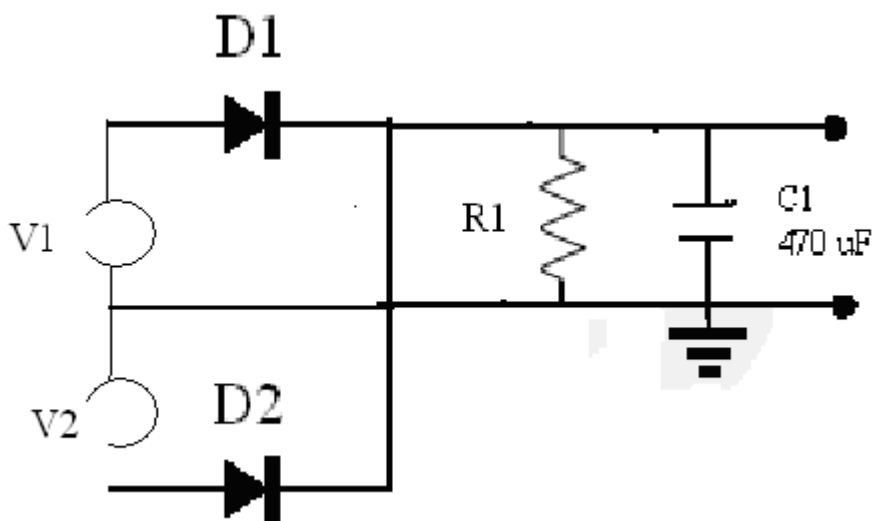


Figure2: Full Wave Rectifier

PROGRAMS:

Half Wave Rectifier

```
v1      1      0      SIN(0 12v 1kHz)
DA      1      2      D1
R       2      0      1k
.MODEL  D1      D
.TRAN   0.1ms   1ms
.PROBE
```

Full Wave Rectifier


```
v1      1      0      SIN(0 12v 60HZ)
v2      0      3      SIN(0 12v 60HZ)
R       2      0      1K
D1      1      2      DA
D2      3      2      DA
.MODEL  DA      D
.TRAN   0.1ms   25ms
.PROBE
```

Result :

2. Verification CE Amplifier

AIM: To Verify the characteristics of CE Amplifier.

CIRCUIT DIAGRAM:

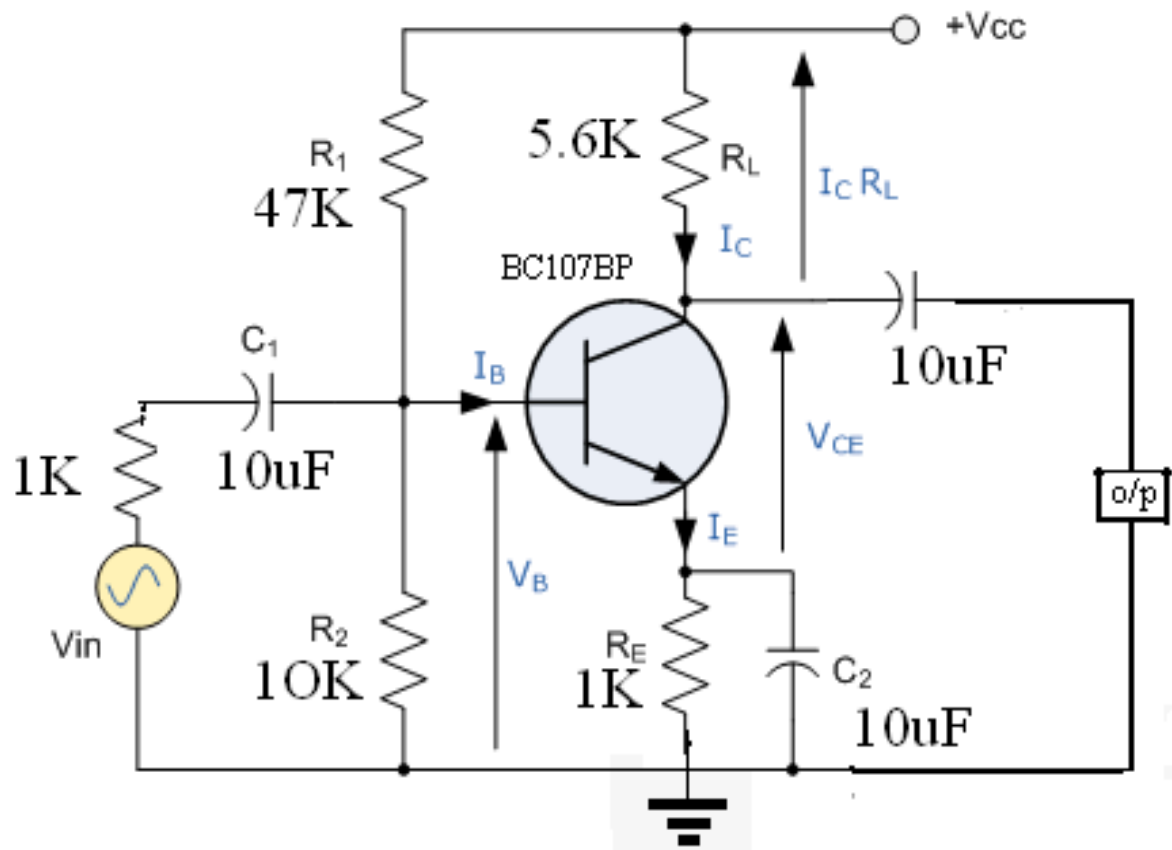

PROGRAM FOR FREQUENCY RESPONSE:

```

vs      1      0      AC      1mv
vcc     4      0      20v
rs      1      2      1k
r1      4      3      40K
r2      3      0      10K
rc      4      5      4K
re      6      0      2K
rl      7      0      2.2K
cs      2      3      10uf
ce      6      0      20uf
cc      5      7      1uf
q1      5      3      6      Q2N2222
c1      5      3      15pf
c2      3      6      3pf
.AC      DEC      10      10      1000K
.MODEL      Q2N2222      NPN(BF=100)
.PLOT      AC      V(7,0)      V(1,0)
.PROBE

```

PROGRAM FOR TRANSIENT ANALYSIS:

```

vs      1      0      SIN(0 1mv 60HZ)
vcc     4      0      20v
rs      1      2      1k
r1      4      3      40K
r2      3      0      10K
rc      4      5      4K
re      6      0      2K
rl      7      0      2.2K
cs      2      3      10uf
ce      6      0      20uf
cc      5      7      1uf
q1      5      3      6      Q2N2222
c1      5      3      15pf
c2      3      6      3pf
.AC      LIN      1      100HZ      100HZ
.PRINT      AC      I(r1)
.MODEL      Q2N2222      NPN(BF=100)

```




```
.TRAN      0.1ms      50ms  
.PROBE  
.END
```

Result :

3. CLASS A POWER AMPLIFIER

AIM: To verify the characteristics of Class A power Amplifier.

CIRCUIT DIAGRAM:

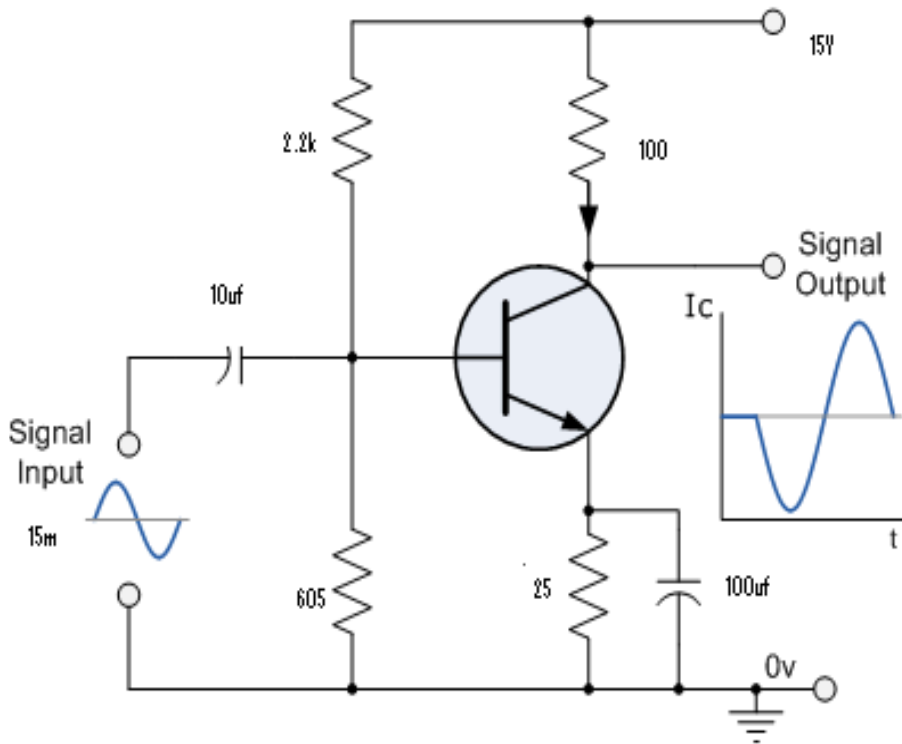

PROGRAM FOR CLASS A POWER AMPLIFIER:

```

VS      1      0      SIN(0 1mv 10KHZ)
VCC     5      0      15V
CB      1      2      10UF
CC      3      6      10UF
CE      4      0      100UF
R1      5      2      2.7K
R2      2      0      605
RC      5      3      100
RE      4      0      25
RL      6      0      47
Q1      3      2      4      SL100
    
```


```
.MODEL      SL100      NPN
.TRAN      0.1ms      0.5ms
.PROBE
.END
```

RESULT:

4. WEIN BRIDGE OSCILLATOR

AIM: TO VERIFY THE CHARACTERISTICS OF WEIN BRIDGE OSCILLATOR

CIRCUIT DIAGRAM:

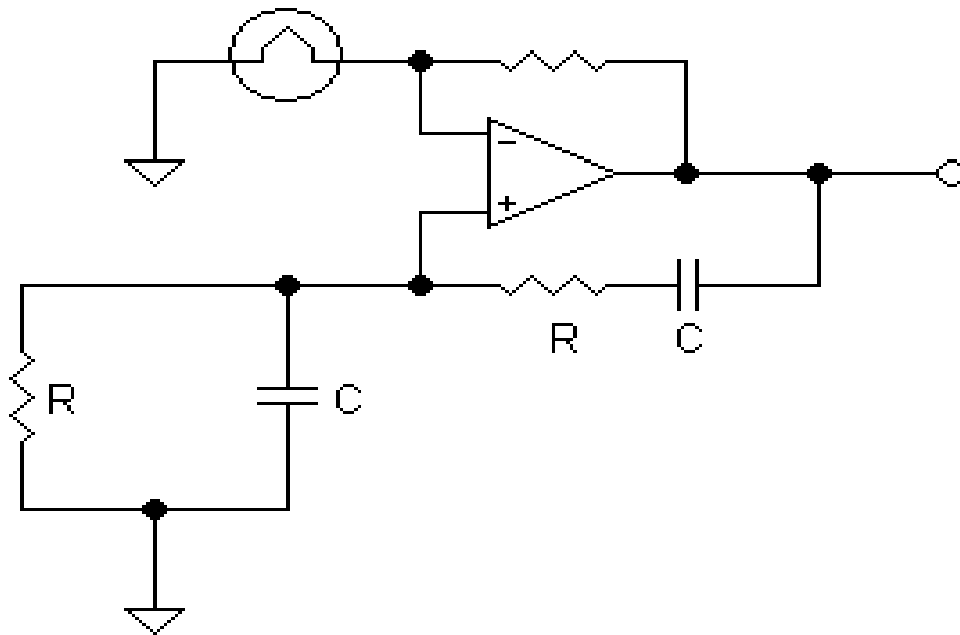


PROGRAM:

```
E          2          0          4          1          2E5
RI          4          1          1E6
RG          1          0          10K
R1          3          4          6366
R2          4          0          6366
RF          2          1          20K
C1          2          3          1NF          IC=2
C2          4          0          1NF
.TRAN      0.05us      50us      UIC
.PROBE
```

5. COMMON SOURCE AMPLIFIER

AIM: To Verify the characteristics of CS Amplifier.

CIRCUIT DIAGRAM:

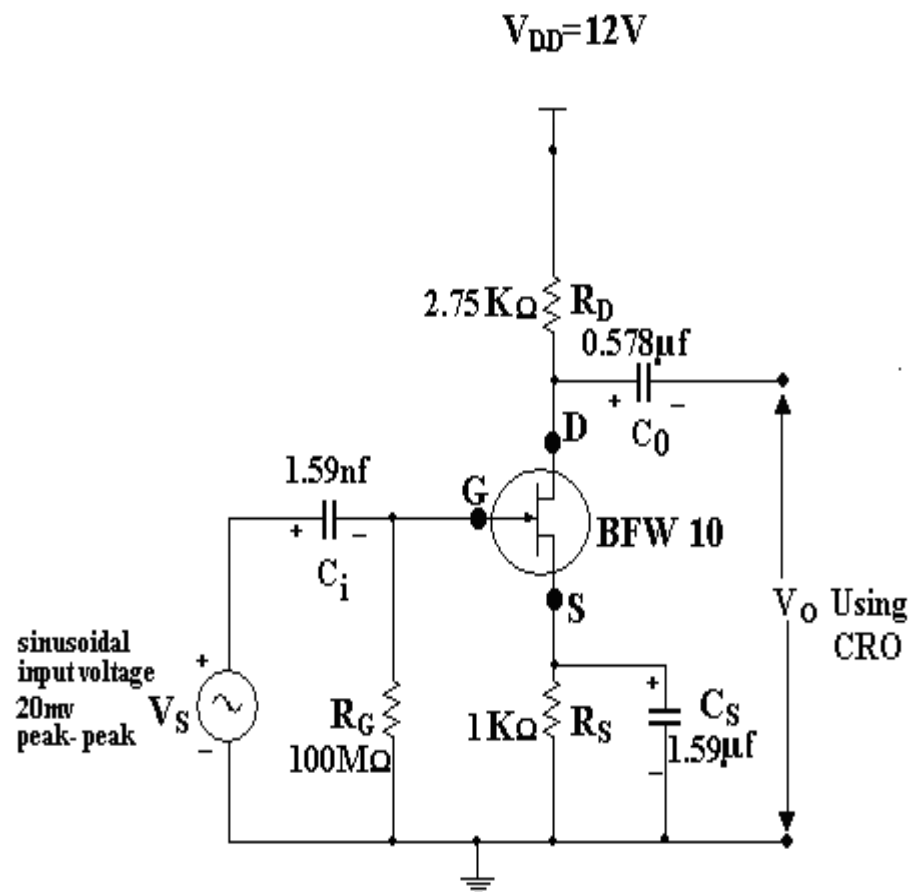

PROGRAM :

CS AMP

```

vs      1      0      ac      20mv
R       2      0      100M
cg      1      2      1.59uf
R1      2      0      100K
R2      2      5      1MEG
Rs      4      0      1K
Rd      3      5      2.75K
VDD     5      0      15v
Cd      3      6      15uf
Cs      4      0      50uf
RL      6      0      20K
jn      3      2      4      BFW10
.MODEL  BFW10  njf
.AC      DEC      10      10      10MEG
.PLOT    AC      V(6,0)  V(1,0)
.PROBE
.END

```

```

vs      1      0      SIN(0  10mv  5KHZ)
R       1      7      15K
cg      7      2      4.7uf
R1      2      0      100K
R2      2      5      1MEG
Rs      4      0      1.5K
Rd      3      5      4.7K
VDD     5      0      15v
Cd      3      6      15uf
Cs      4      0      50uf
RL      6      0      20K
jn      3      2      4      BFW10
.MODEL  BFW10  njf
.TRAN   0.1ms   0.6ms
.PROBE
.END

```