

# VHDL AND CAD Laboratory (EC-452) Lab Manual

Prepared by  
**Y.Sri Chakrapani, M.Tech**  
(Lecturer)  
&  
**S.K.M.Subhani, M.Tech**  
(Lecturer)



*DEPARTMENT OF ECE*  
*BAPATLA ENGINEERING COLLEGE*  
*BAPATLA*

## **LIST OF EXPERIMENTS**

1. LOGIC GATES	2
2. MODULO SYNCHRONOUS UP-DOWN COUNTER	11
3. MULTIPLERXERS/DECODERS	13
4. DESIGN OF ALU	17
5. PRIORITY ENCODER	19
6. 4-BIT MAGNITUDE COMPARATOR	21
7. PARITY GENERATOR	23
8. LINEAR CONVOLUTION	25
9. CIRCULAR CONVOLUTION	26
10. AUTO-CORRELATION	28
11. CROSS-CORRELATION	30
12. FFT USING DIF	31
13. IFFT USING DIF	33
14. FFT USING DIT	34
15. IFFT USING DIT	36
16. DESIGN OF BUTTER WORTH FILTER USING IMPUSEINVARIANT METHOD	37
18 DESIGN OF LPF USING HAMMING WINDOWS	38
19. DFT	39

## 1.LOGIC GATES

### 1.1 AND GATE

#### Aim:

To implement And Gate using VHDL.


#### Code:

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;


entity and1 is
    port(A,B : in std_logic;
         C : out std_logic);
end and1;

architecture archi of and1 is
begin
    C <= A and B;
end archi;
```

#### RTL SCHEMATIC:

 

#### Simulation Waveforms

 

## 1.2 OR GATE

### Aim:

To implement And Gate using VHDL.

### Code:

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;


entity or1 is
    port(A,B : in std_logic;
         C : out std_logic);
end or1;

architecture archi of or1 is
begin
    C <= A or B;
end archi;
```

### RTL Schematic:



### Simulation Waveforms:

 

## 1.3 NAND GATE

Aim:

To implement Nand Gate using VHDL.

Code:

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;


entity nand1 is
    port(A,B : in std_logic;
         C : out std_logic);
end nand1;

architecture archi of nand1 is
begin
    C <= A nand B;
end archi;
```

RTL Schematic:



Simulation Waveforms:

 

### Aim:

To implement Nand Gate using VHDL.


### Code:

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;


entity exor1 is
    port(A,B : in std_logic;
         C : out std_logic);
end exor1;

architecture archi of exor1 is
begin
    C <= A xor B;
end archi;
```

### RTL Schematic:

 

### Simulation Waveforms:

 

### Aim:

To implement Not Gate using VHDL.

### Code:

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;


entity exor1 is
    port(A : in std_logic;
         B : out std_logic);
end exor1;

architecture archi of exor1 is
begin
    B<= not A;
end archi;
```

### RTL Schematic:



### Simulation Waveforms:

 

## **1.6 HALF ADDER**

### Aim:

To implement Half Adder using VHDL.

### Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;


entity halfadder is
    port(
        a    : in  std_logic;
        b    : in  std_logic;
        s    : out std_logic;
        cout : out std_logic);
end halfadder;

architecture Behavioral of halfadder is

begin
    s <= a xor b;
    cout <= a and b;


end Behavioral;
```

### RTL Schematic:

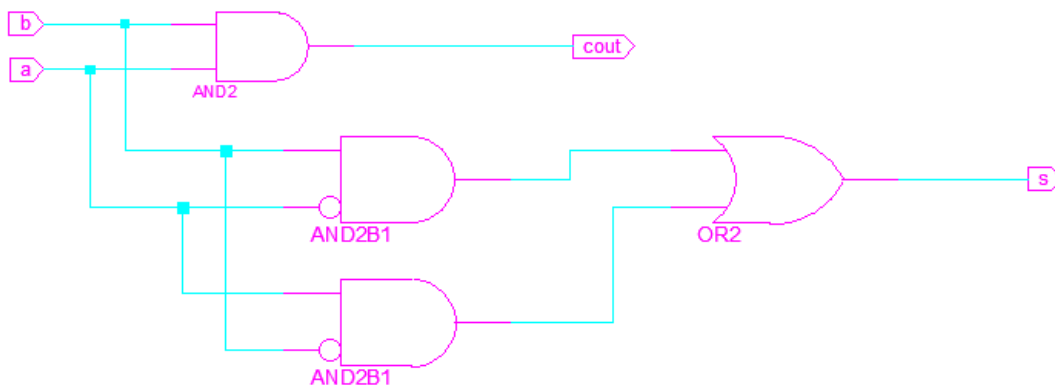



### Simulation Waveforms:

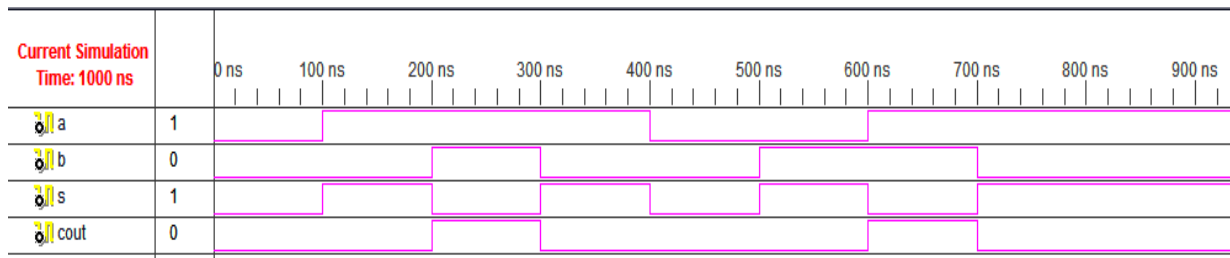

## 1.7 FULL ADDER

### Aim:

To implement Full Adder using VHDL.

### Code:

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```


```

ENTITY full_adder IS
    PORT(x:      IN    std_logic ;
          y:      IN    std_logic ;
          cin:    IN    std_logic ;
          cout:   OUT   std_logic ;
          sum:    OUT   std_logic
    ) ;
END full_adder ;


ARCHITECTURE equations OF full_adder IS
BEGIN
    sum  <= x XOR y XOR cin ;
    cout <= (x AND y) OR (x AND cin) OR (y AND cin) ;
END ;

```

### RTL Schematic:

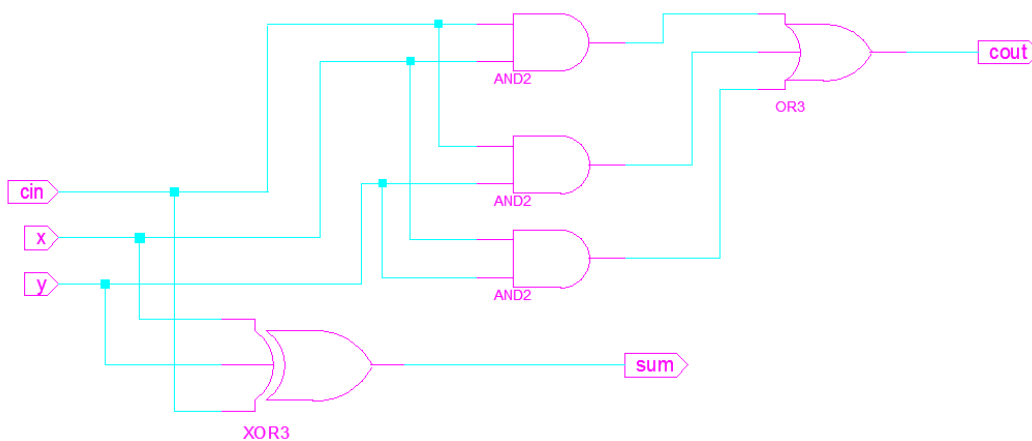

### Simulation waveforms:

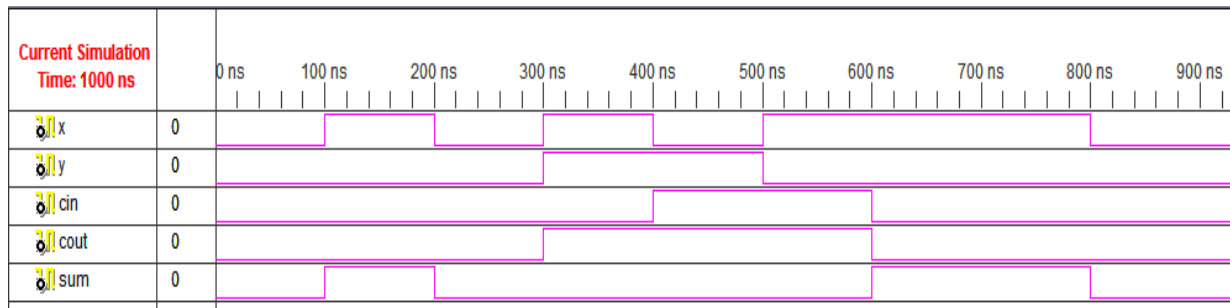

## **2. MODULO SYNCHRONOUS UP-DOWN COUNTER**

### Aim:

To implement Modulo Synchronous Up-Down Counter using VHDL.

### Code:

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_unsigned.all;
```


```

entity counter is
    port(C, CLR, UP_DOWN : in std_logic;
          Q : out std_logic_vector(3 downto 0));
end counter;


architecture archi of counter is
    signal tmp: std_logic_vector(3 downto 0);
begin
    process (C, CLR)
    begin
        if (CLR='1') then
            tmp <= "0000";
        elsif (C'event and C='1') then
            if (UP_DOWN='1') then
                tmp <= tmp + 1;
            else
                tmp <= tmp - 1;
            end if;
        end if;
    end process;
    Q <= tmp;
end archi;

```

### RTL Schematic:

 

### Simulation Waveforms:

 

### 3.1 MULTIPLEXER 8x1

#### Aim:

To implement Multiplexer 8x1 using VHDL.

#### Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```

entity mux8x1 is
    Port (
        i : in std_logic_vector(7 downto 0);
        s : in std_logic_vector (2 downto 0);
        y : out std_logic
    );
end mux8x1;

architecture Behavioral of mux8x1 is


begin

    process (i,s)
    begin
        if (s = "000") then y <= i(0);
        elsif (s = "001") then y <= i(1);
        elsif (s = "010") then y <= i(2);
        elsif (s = "011") then y <= i(3);
        elsif (s = "100") then y <= i(4);
        elsif (s = "101") then y <= i(5);
        elsif (s = "110") then y <= i(6);
        else y <= i(7);
        end if;
    end process;


end Behavioral;

```

RTL Schematic:

 

### Simulation Waveforms:

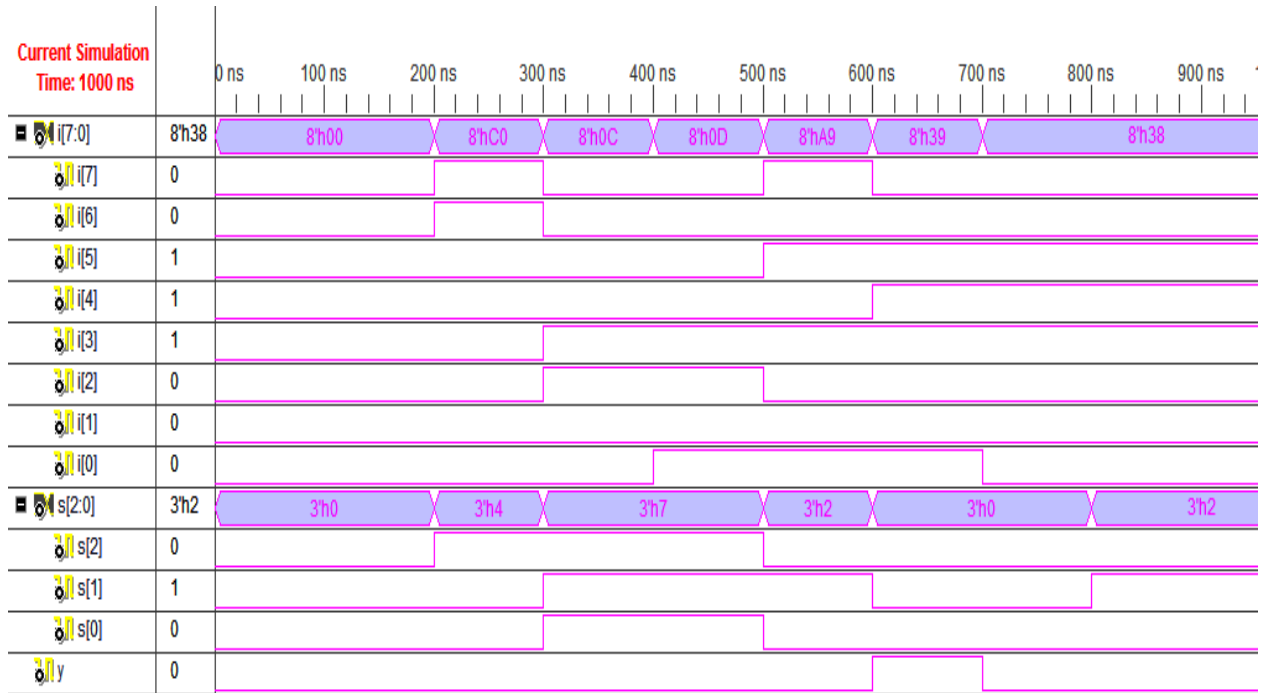

### 3.2 DECODER 2x4

#### Aim:

To implement Decoder 2x4 using VHDL.

#### Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity decoder2x4 is
```

```
port (sel: in std_logic_vector (1 downto 0);  
      e: in std_logic;  
      y: out std_logic_vector (3 downto 0));
```

```
end decoder2x4;
```


architecture Behavioral of decoder2x4 is  
begin

```
    process(e,sel)  
    begin  
        if(e='0') then  
            if(sel = "00") then  
                y <= "0111" ;  
            elsif(sel = "01") then  
                y <= "1011" ;  
            elsif(sel = "10") then  
                y <= "1101" ;  
            else  
                y <= "1110" ;  
            end if;  
        else  
            y <= "1111";  
        end if;  
    end process;
```


```
end Behavioral;
```

RTL Schematic:



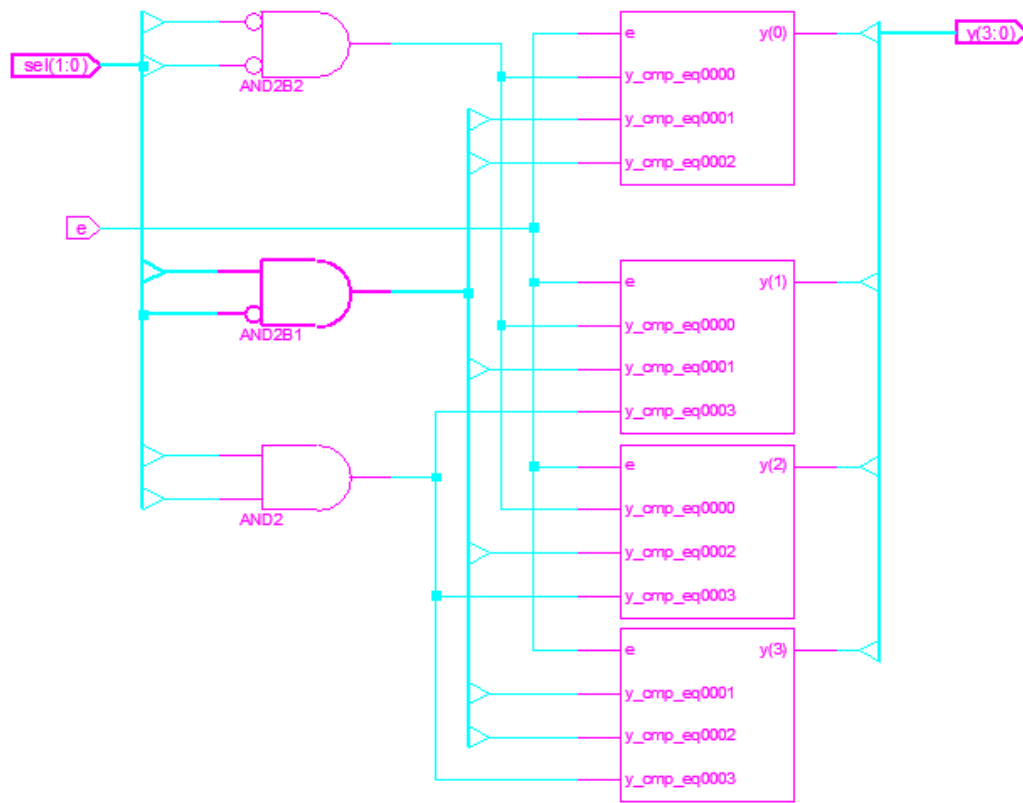

#### Simulation Waveforms:

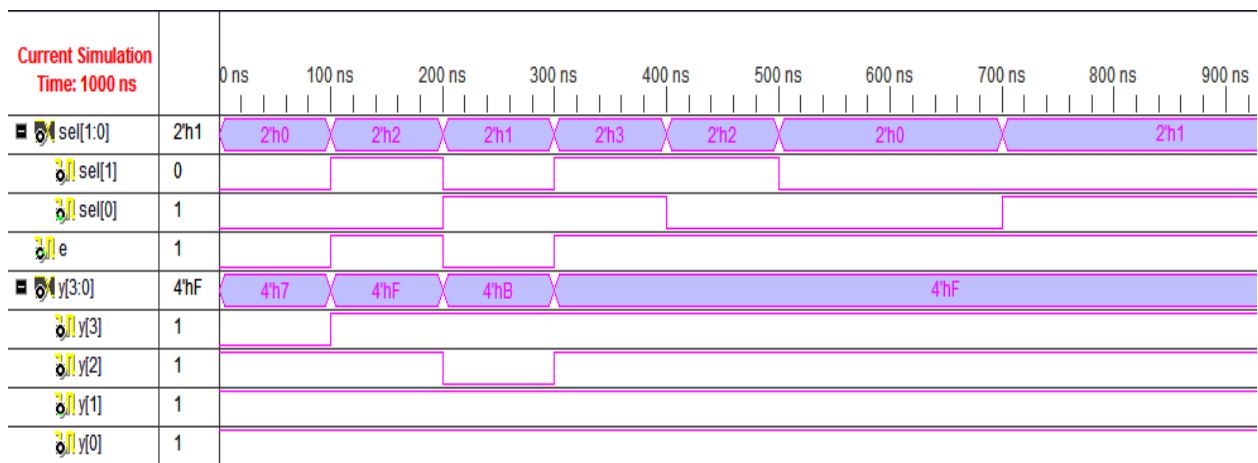

#### 4.DESIGN OF ALU

Aim:

To implement 4-Bit ALU using VHDL.

Code:


```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
use IEEE.std_logic_arith.all;

entity LC2_ALU is
    port( A: in std_logic_vector (3 downto 0);
          B: in std_logic_vector (3 downto 0);
          S: in std_logic_vector (3 downto 0);
          Y: out std_logic_vector (3 downto 0));
end LC2_ALU;

architecture bhv of LC2_ALU is
begin
    process(A, B, S)
    begin

        case S is
            when "0000" => Y <= A or B;
            when "0001" => Y <= A and B;
            when "0010" => Y <= A;
            when "0011" => Y <= not A;
            when "0100" => Y <= A xor B;
            when "0101" => Y <= A nand B;
            when "0110" => Y <= A + B;
            when "0111" => Y <= A - B;
            when "1000" => Y <= A*B;
            when "1001" => Y <= A/B;
            when others => null;
        end case;

    end process;
end bhv;
RTL Schematic:
```

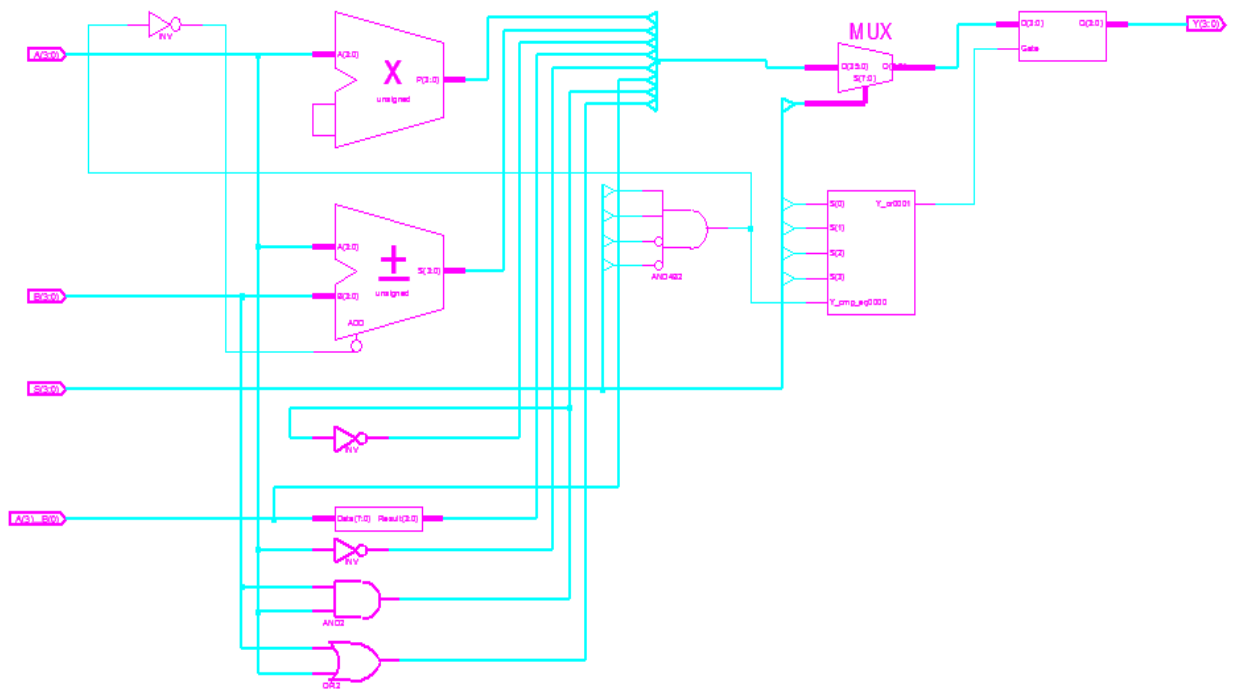

Simulation Waveforms:

Current Simulation Time: 1000 ns		0 ns	100 ns	200 ns	300 ns	400 ns	500 ns	600 ns	700 ns	800 ns	900 ns
a[3:0]	4'hC	4'h0	4'hE	4'h8	4'h2	4'h6	4'h4	4'hC			
b[3:0]	4'hE	4'h0	4'h8	4'hC	4'h9	4'hB	4'hF	4'hE			
s[3:0]	4'h3	4'h0	4'h8	4'h4	4'h6	4'h7	4'h3				
y[3:0]	4'h3	4'h0	4'h7	4'h4	4'hB	4'h9	4'h3				

## 5. PRORITY ENCODER

Aim:

To implement Priority Encoder 4x2 using VHDL.

Code:

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;

entity priority_encoder4x2 is
    Port (      i : in std_logic_vector(3 downto 0);
            y : out std_logic_vector(1 downto 0)
    );
end priority_encoder4x2;


architecture Behavioral of priority_encoder4x2 is

begin


    process (i)
    begin
        if (i = "0000") then
            y <="XX";
        else
            if (i = "0001")or (i = "1111") then y <=
"11";
            elsif (i = "0010")or (i = "1110")    then
y <= "10";
            elsif (i = "0100")or (i = "1100")    then
y <= "01";
            elsif (i = "1000")                    then y <=
"00";
            end if;
        end if;

    end process;
end Behavioral;
```

RTL Schematic:

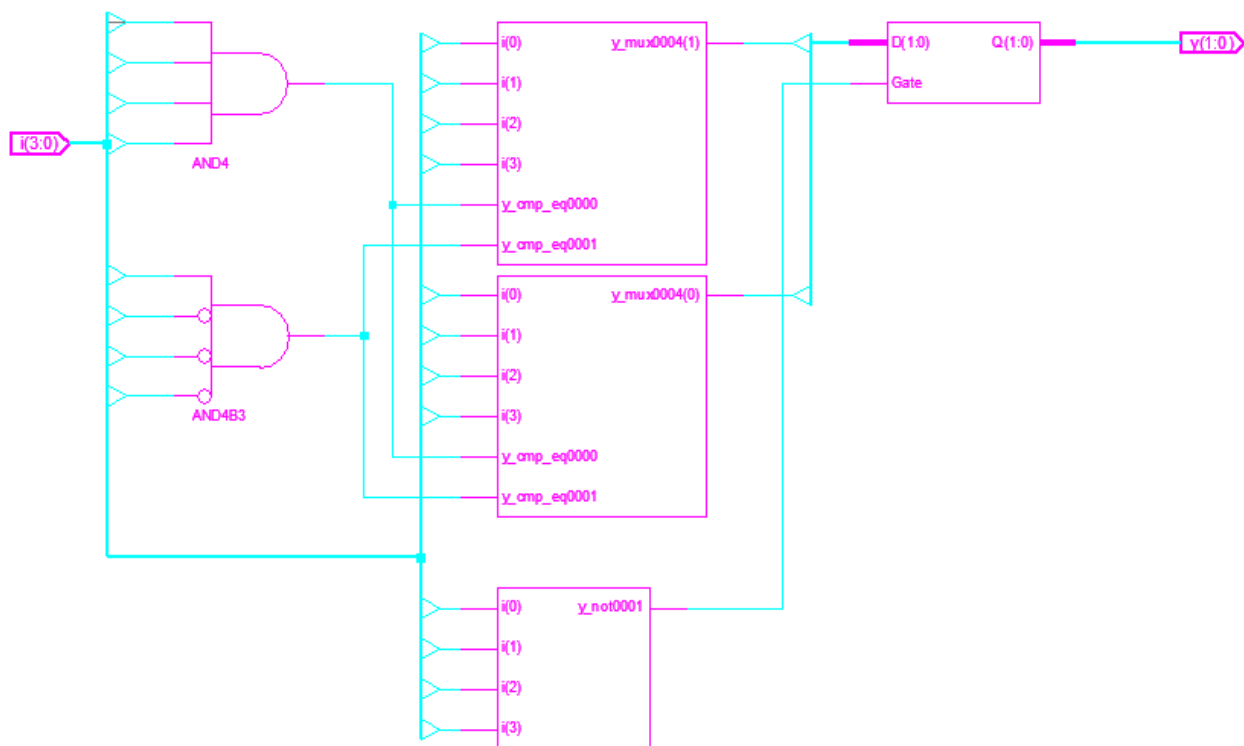

### Simulation Waveforms:

 

## 6. MAGNITUDE COMPARATOR

Aim:


To implement 4-Bit Magnitude Comparator using VHDL.

Code:

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;


ENTITY compare IS
    PORT ( A, B : IN STD_LOGIC_VECTOR(3 DOWNT0 0) ;
          AeqB, AgtB, AltB : OUT STD_LOGIC ) ;
END compare ;

 ARCHITECTURE Behavior OF compare IS
BEGIN
    AeqB <= '1' WHEN A = B ELSE '0' ;
    AgtB <= '1' WHEN A > B ELSE '0' ;
    AltB <= '1' WHEN A < B ELSE '0' ;
END Behavior ;
```



RTL Schematic:

## Simulation Waveforms:

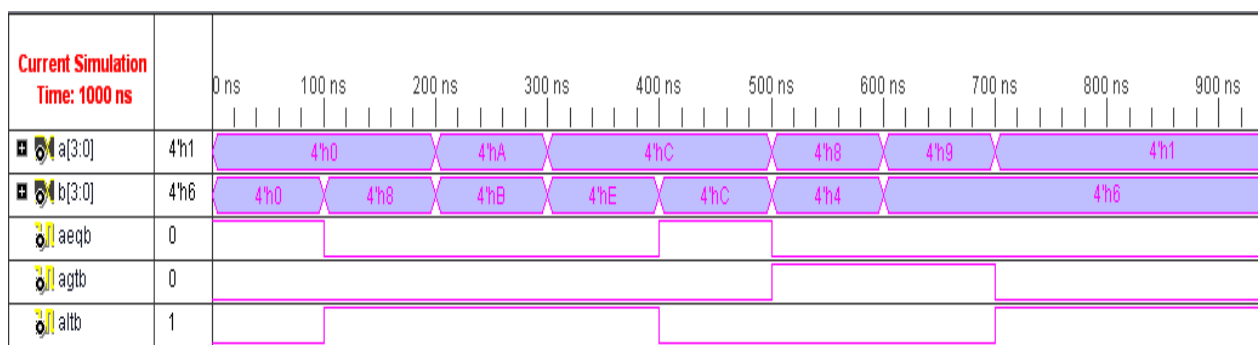

## 7. PARITY GENERATOR

Aim:

To implement 4-Bit Parity Generator using VHDL.

Code:


```
LIBRARY ieee;
USE ieee.std_logic1164.ALL;

ENTITY parity4_gen IS
PORT(d : IN STD_LOGIC_VECTOR (0 to3);
      pe : OUT STD_LOGIC);
END parity4_gen;


ARCHITECTURE parity OF parity4_gen IS
    SIGNAL p : STD_LOGIC_VECTOR (1 to 3);
BEGIN
    p(1) <= d(0) xor d(1);
    FOR i IN 2 to 3 GENERATE
        p(i) <= p(i-1) xor d(i);
    END GENERATE;
    pe <= p(3);
END parity;
```

RTL Schematic:



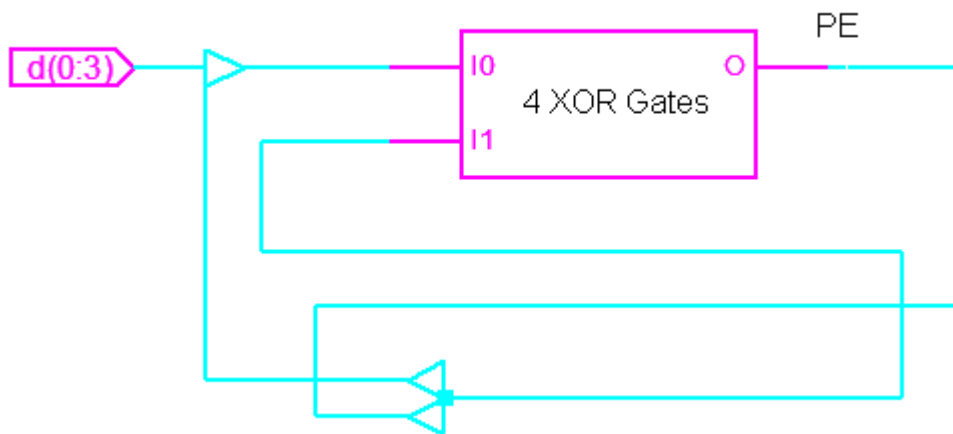

### Simulation Waveforms:

 

## 8.LINEAR CONVOLUTION

```
x=input ('Enter first sequence;')
h=input ('Enter Second sequence;')
m=length(x);
n=length (h);
l=m+n-1;

for i=1:l
    r(i)=0;
end

for k=1:l
    for j=max(1,k+1-n):min(k, m)
        r(k)=r(k)+x(j)*h(k+1-j);
    end
end

.....

Enter first sequence; [1 2 3]
Enter Second sequence; [1 2 3 4]

r = [ 1      4      10      16      17      12]
```

## 9.CIRCULAR CONVOLUTION

```
a=input('Enter first sequence:');
b=input('Enter Second sequence:');
x=length(a);
y=length(b);
z=max(x,y);
if x>y
for i=y+1:x
    b(i)=0;
end
elseif x<y
    for j=x+1:y
        a(j)=0
    end
end
for i=1:z
    c(i)=0;
    for k=1:z
        j=(i-k)+1;
```

```
    if (j<=0)
        j=z+j;
    end
    c(i)=c(i)+(a(k)*b(j));
end
end
.....
```

Enter first sequence: [1 2 2 2]

Enter Second sequence: [1 2 3]

c =[ 11 10 9 12]

## 10.AUTO-CORRELATION

```
a=input('Enter the sequence:');  
n1=length (a);  
n=2*n1-1;  
b=zeros(1,n);  
c=zeros(1,n);  
d=zeros(1,n);  
n2=n-n1;  
for i=1:n1  
b(i)=a(i);  
end  
for i=n2:n-1  
c(i+1)=a(i+1-n2);  
end  
for i=1:n  
d(i)=sum(b.*c);  
for j=n:-1:2  
b(j)=b(j-1);  
end
```

```
b(i)=0;  
end  
Enter first sequence: [1 2 3 4]  
  
Ans = [4 11 20 30 20 11 4]
```

## 11. CROSS-CORRELATION

```
x=input('Enter first sequence:');
h1=input('Enter Second sequence:');
m=length(x);
n=length(h1);
h(n:-1:1)=h1(1:n);
l=m+n-1;
for i=1:l
    r(i)=0;
end
for k=1:l
    for j=max(1,k+1-n):min(k,m)
        r(k)=r(k)+x(j)*h(k+1-j);
    end
end
.....
Enter first sequence:[1 2 2 2]

Enter Second sequence:[2 2 3]

ans: r =[ 3      8      12      14      8      4]
```

## 12.FFT USING DIF

```
function a=difffft(a)
N=length(a);
l=log2(N);
for m=1:-1:1
for t=0:1:(2^(m-1))-1
    k(t+1)=(N*t)/2^m;
    wn(t+1)=exp((-2*i*pi*k(t+1))/N);
end
for p=1:2^m:(N-2^(m-1))
    r=1;
    x=p;
    for q=x+2^(m-1):1:(x+2^m)-1
        b(p)=a(p)+a(q);
        b(q)=(a(p)-a(q))*wn(r);
        p=p+1;
        r=r+1;
    end
end
end
```



```
a=b;
```

```
end
```

```
a=bitrevorder(a);
```

```
return;
```

```
.....
```

```
a=[1 2 3 4]
```

```
X=fftdif(a)
```

```
x = 10.0000 -2.0000 + 2.0000i -2.0000  
-2.0000 - 2.0000i
```

### 13.IFFT USING DIF

```
function r =idftdif(a)
```

```
a=conj(a);
```

```
a=difffft(a);
```

```
a=(a/length(a));
```

```
r=conj(a);
```

```
return;
```

```
.....
```

```
A = 10.0000          -2.0000 + 2.0000i  -2.0000  
-2.0000 - 2.0000i
```

```
r =idftdif(a)
```

```
a=[1  2  3  4]
```

#### 14.FFT USING DIT

```
function b=ditfft(a)

a=bitrevorder(a);

N=length(a);

l=log2(N);

for m=1:l

for t=0:1:(2^(m-1))-1

    k(t+1)=(N*t)/2^m;

    wn(t+1)=exp((-2*i*pi*k(t+1))/N);

end

for p=1:2^m:(N-2^(m-1))

    r=1;

    x=p;

    for q=x+2^(m-1):1:(x+2^m)-1

        b(p)=a(p)+a(q)*wn(r);

        b(q)=a(p)-a(q)*wn(r);

        p=p+1;

        r=r+1;

    end

end
```

```
end
```

```
end
```

```
return;
```

```
.....
```

```
a=[1 2 2 2]
```

```
b=ditfft(a)
```

```
b=[7      -1      -1      -1]
```

## 15.IFFT USING DIT

```
function a =idftdit(a)
```

```
a=conj(a);
```

```
a=ditfft(a);
```

```
a=(a/length(a));
```

```
a=conj(a);
```

```
return;
```

```
-----  
-----
```

```
a=[7 -1 -1 -1];
```

```
b=idftdit(a)
```

```
b= 1      2      2      2
```

## 16. DESIGN OF BUTTERWORTH FILTER USING IMPULSEINVARIANT METHOD

```
function [b,a] =butteriit(wp,ws,ap,as,t);
```

```
p=(10^(0.1*ap)-1)^0.5;
```

```
s=(10^(.1*as)-1)^0.5;
```

```
n=ceil(log(p/s)/log(wp/ws));
```

```
wc=wp/(p^(1/n)*t);
```

```
[u,v]=butter(n,wc,'s');
```

```
[r,p,k]=residue(u,v);
```

```
p=exp(p*t);
```

```
[b,a]=residue(r,p,k)
```

```
-----  
[b,a] =butteriit(.2*pi,.3*pi,7,16,1)
```

```
a =
```

```
    1.0000    -2.0233    1.4675   -0.3690
```

```
b =
```

```
    0    0.0438    0.0314
```

## 17.DESIGN OF LPF USING HAMMING WINDOW

```

Function    hamm(wp,ws)
T=ws-wp;
wc=ws-wp;
wc=(ws+wp)/2;
M=ceil(6.6*pi/t)+1;
hd=ideal-lp(wc,M);
function hd=ideal-lp(wc,M)
x=(M-1)/2;
n=[0:M-1];
m=n-x+eps;
hd=sine(wc*m)./(pi*m);
for i=1:m
w-ham(1)=0.54-.46*cos(2*pi*( )i-1)/M;
end
M=hd.*w-ham;
subplot(2,2,1);stem(h,hd);titll('Ideal Imp
Responce');
axis([0 M-1-.1 0.4]);Xlable('n');Ylble('hd(n));
subplot(2,2,2);steam(n,w-ham);
title('Hamming window')
axis([0 M-1 0 1.1]);Xlable('n');Ylable('hd(n));
subplot(2,2,3);stem(n,H);title('Actual Imp
Responce')
axis([0 N-1 .1 .4]);Xlable('n');
Y lable('H(n)');

```